

## USING OP AMP COMPENSATION PIN FOR CLIPPING

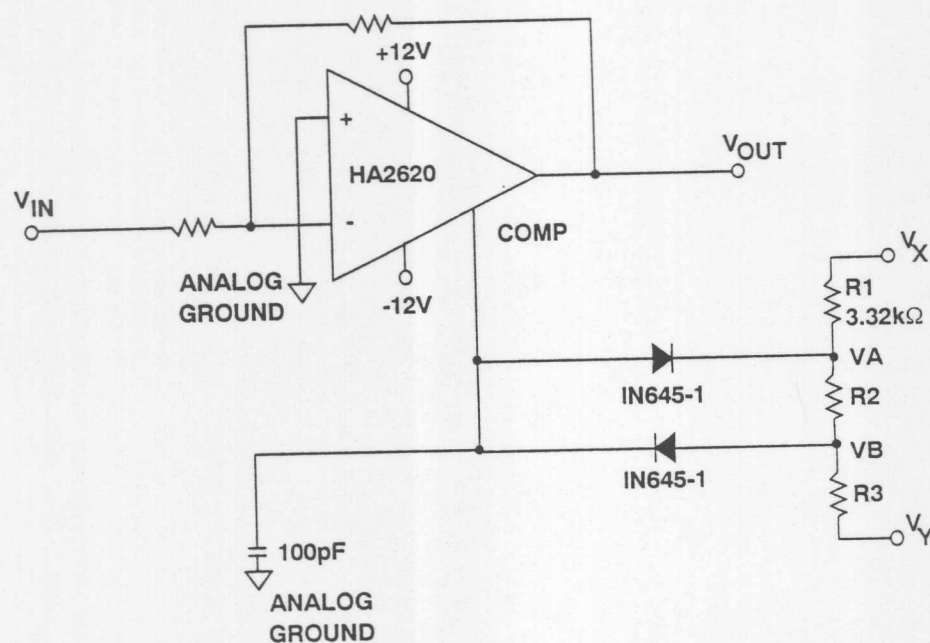


Figure 10.12

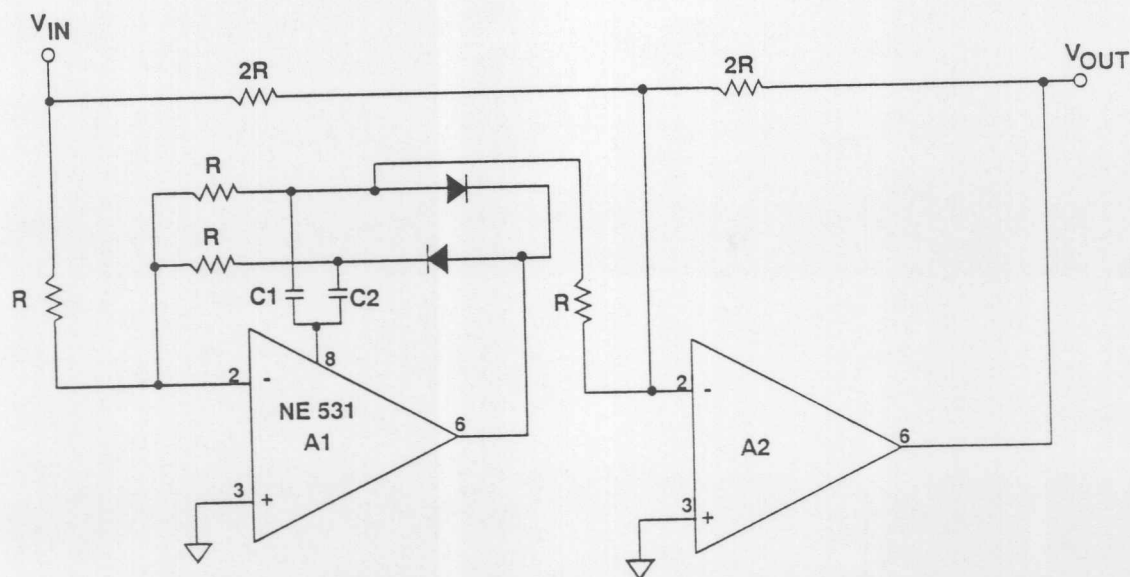
PRECISION FULL-WAVE RECTIFIER  
MINIMIZES ZERO-VOLT "DEADBAND"

Figure 10.13